

Simple Instruction Pipelining

Krste Asanovic
Laboratory for Computer Science
Massachusetts Institute of Technology



Processor Performance Equation

- ☐ Instructions per program depends on source code, compiler technology, and ISA
- ☐ Microcoded DLX from last lecture had cycles per instruction (CPI) of around 7 *minimum*
- ☐ Time per cycle for microcoded DLX fixed by microcode cycle time
 - mostly ROM access + next μPC select logic



Pipelined DLX


To pipeline DLX:

☐ First build unpipelined DLX with CPI=1

□ Next, add pipeline registers to reduce cycle time while maintaining CPI=1



A Simple Memory Model

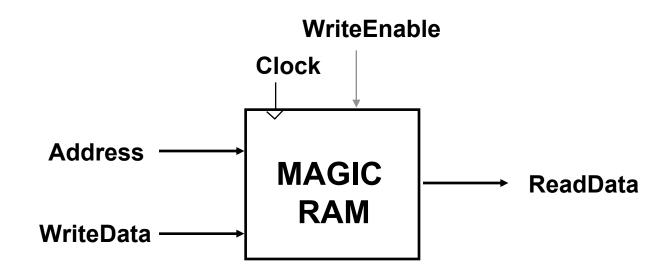


Reads and writes are always completed in one cycle

- a Read can be done any time (i.e. combinational)
- a Write is performed at the rising clock edge if it is enabled
 - ⇒ the write address, data, and enable must be stable at the clock edge



Datapath for ALU Instructions

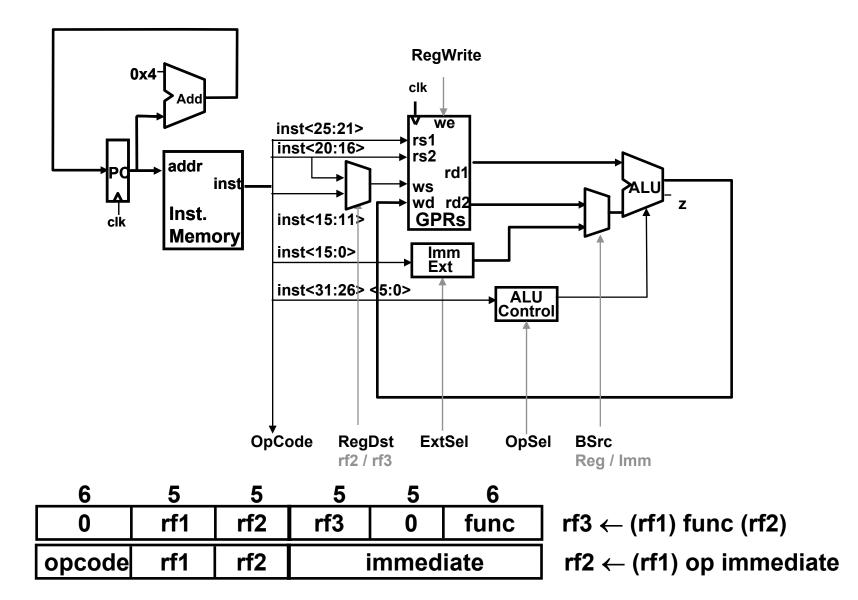



Datapath for Memory Instructions

Should program and data memory be separate?

Harvard style: separate (Aiken and Mark 1 influence)

- read-only program memory
- read/write data memory at some level the two memories have to be the same


Princeton style: the same (von Neumann's influence)

- A Load or Store instruction requires accessing the memory more than once during its execution



Load/Store Instructions:


Harvard-Style Datapath

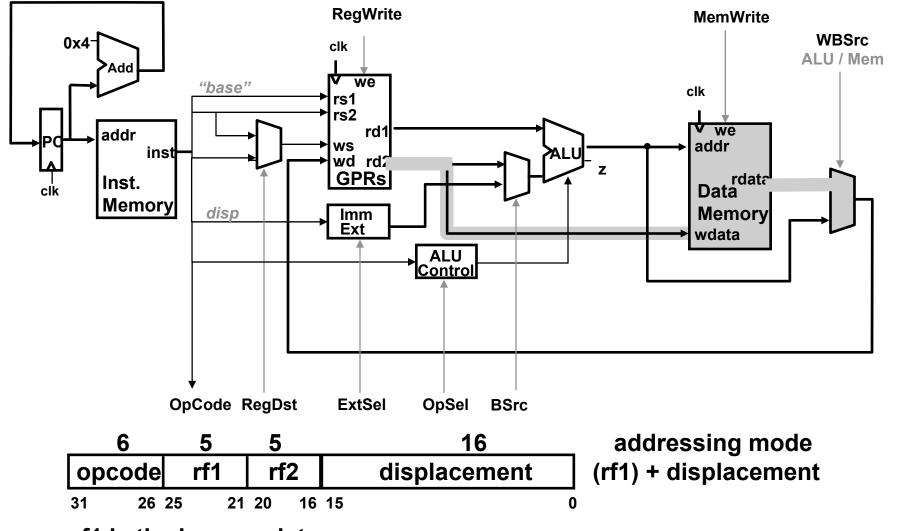

rf1 is the base register rf2 is the destination of a Load or the source for a Store



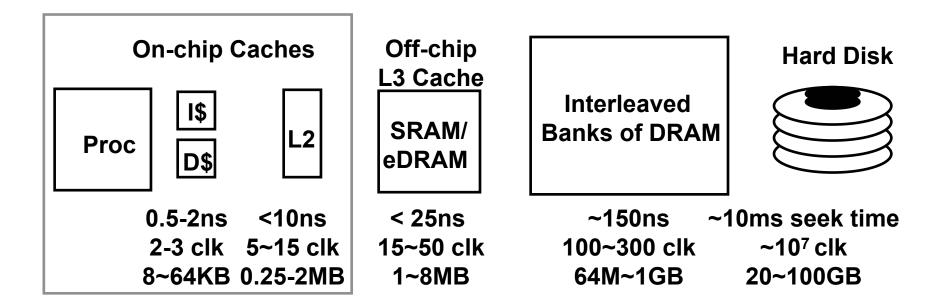
Memory Hierarchy c.2002 Desktop & Small Server



Our memory model is a good approximation of the hierarchical memory system when we hit in the on-chip cache




Conditional Branches

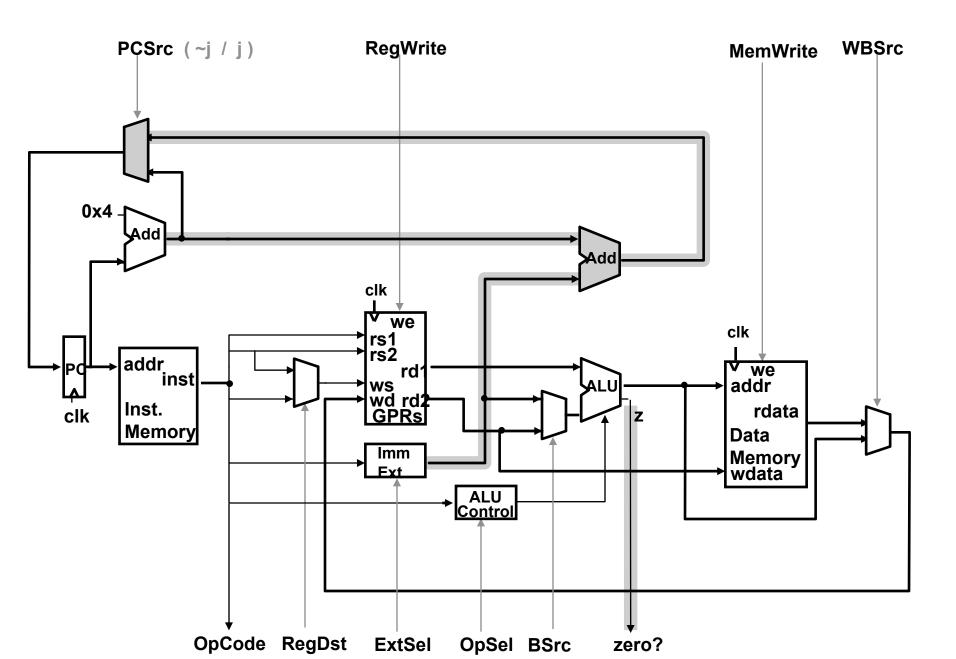




Register-Indirect Jumps

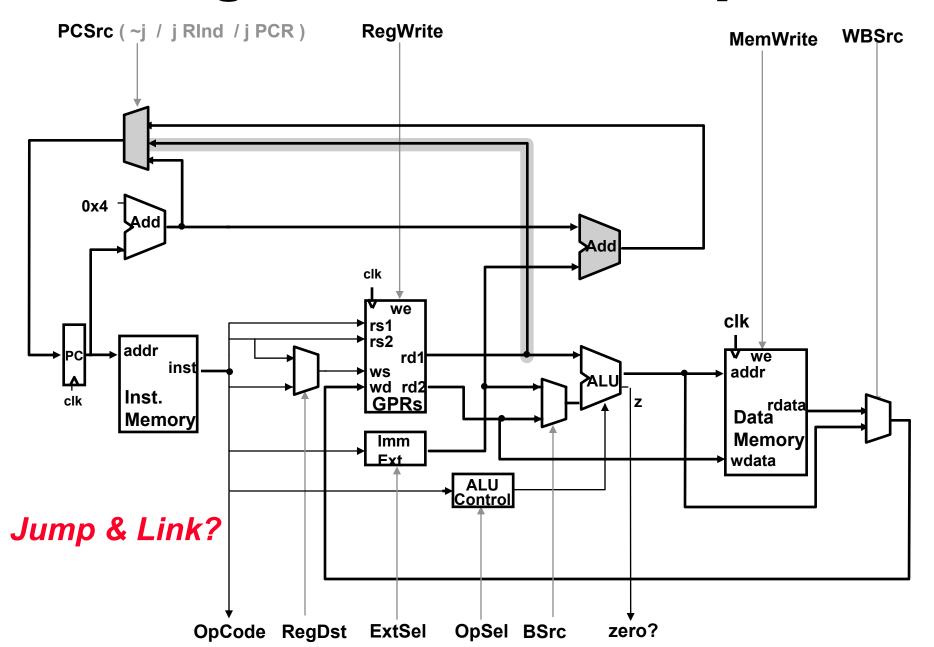




Jump & Link

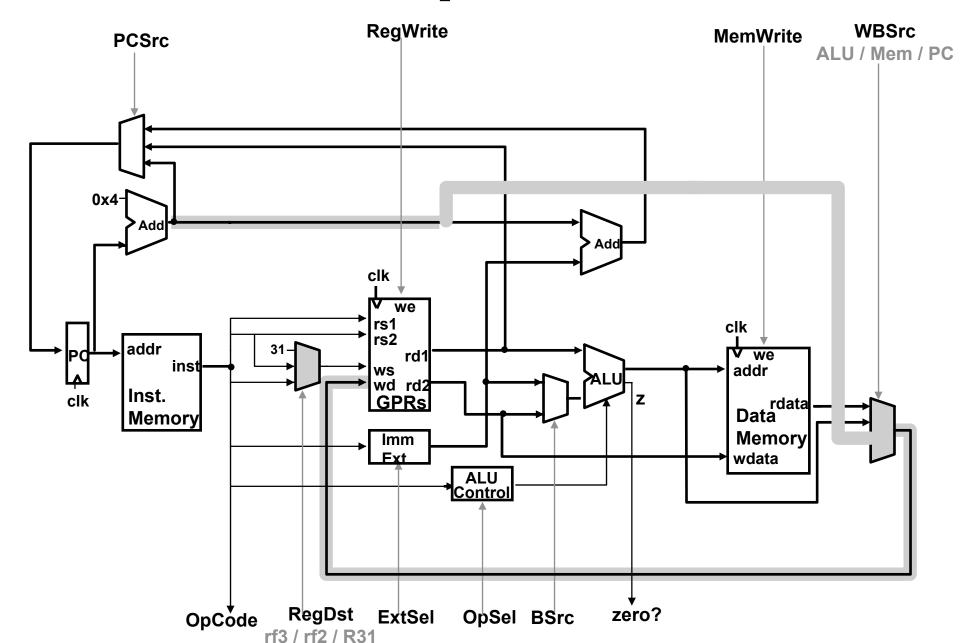




PC-Relative Jumps

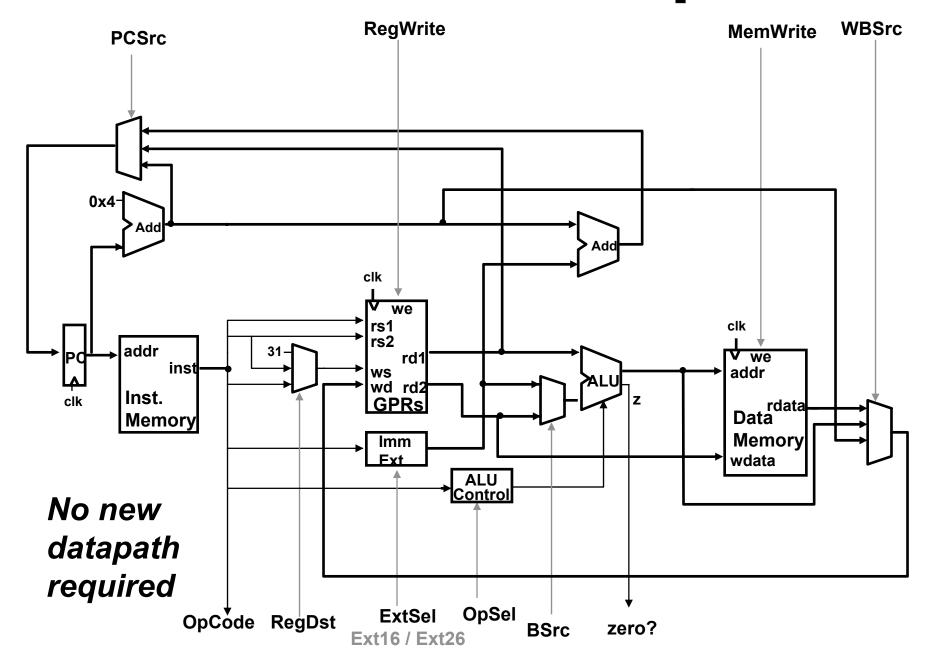




Hardwired Control is pure Combinational Logic:

Unpipelined DLX

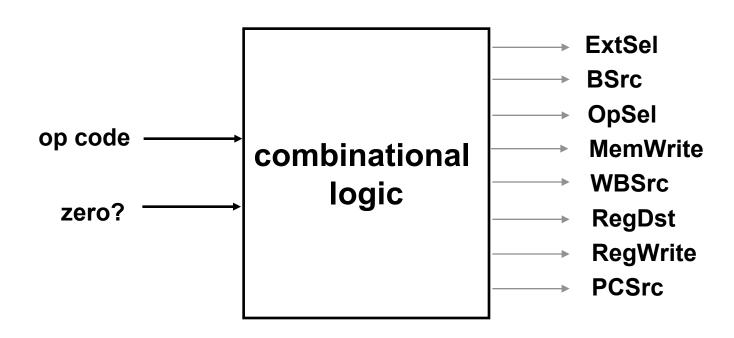




ALU Control & Immediate Extension

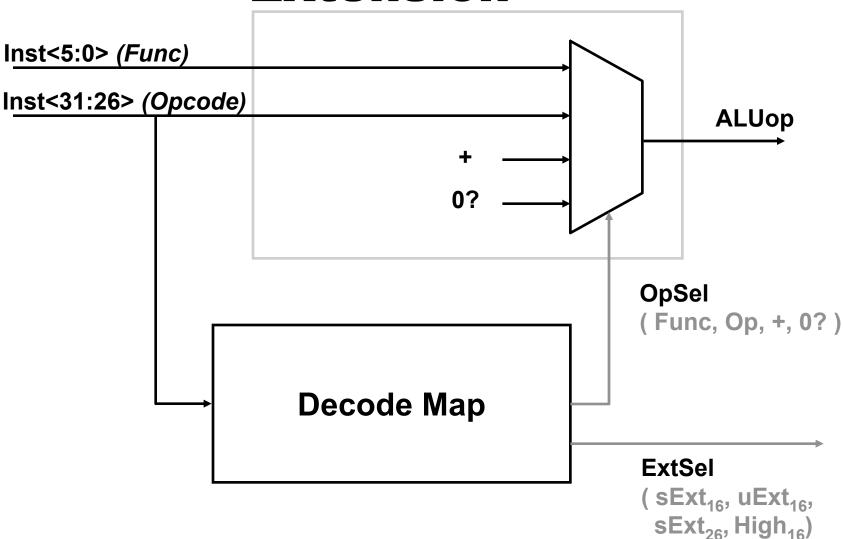



Hardwired Control worksheet

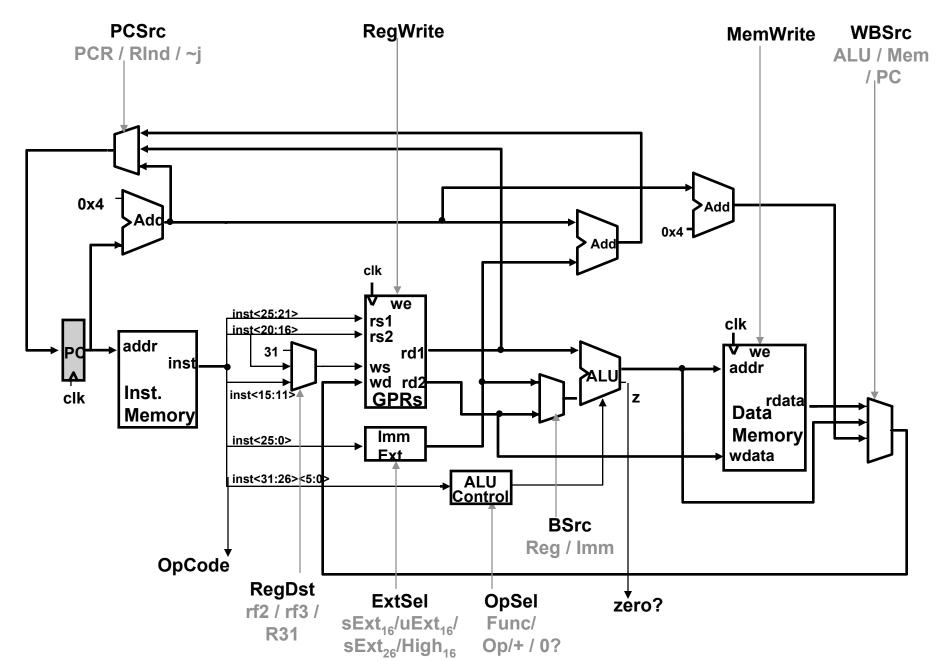



Hardwired Control Table

BSrc = Reg / Imm PCSrc1 = j / ~j WBSrc = ALU / Mem / PC PCSrc2 = PCR / RInd RegDst = rf2 / rf3 / R31

Opcode	Ext Sel	BSrc	Op Sel	Mem Write	Reg Write	WB Src	Reg Dest	PC Src
ALU	*	Reg	Func	no	yes	ALU	rf3	~j
ALUu	*	Reg	Func	no	yes	ALU	rf3	~j
ALUi	sExt ₁₆	lmm	Ор	no	yes	ALU	rf2	~j
ALUiu	uExt ₁₆	lmm	Ор	no	yes	ALU	rf2	~j
LW	sExt ₁₆	lmm	+	no	yes	Mem	rf2	~j
SW	sExt ₁₆	lmm	+	yes	no	*	*	~j
BEQZ _{z=0}	sExt ₁₆	*	0?	no	no	*	*	PCR
BEQZ _{z=1}	sExt ₁₆	*	0?	no	no	*	*	~j
J	sExt ₂₆	*	*	no	no	*	*	PCR
JAL	sExt ₂₆	*	*	no	yes	PC	R31	PCR
JR	*	*	*	no	no	*	*	RInd
JALR	*	*	*	no	yes	PC	R31	RInd



Hardwired Unpipelined Machine

- ☐ Simple
- ☐ One instruction per cycle
- ☐ Why wasn't this a popular machine style?



Unpipelined DLX

Clock period must be sufficiently long for all of the following steps to be "completed":


- 1. instruction fetch
- 2. decode and register fetch
- 3. ALU operation
- 4. data fetch if required
- 5. register write-back setup time

$$\Rightarrow$$
 $t_C > t_{IFetch} + t_{RFetch} + t_{ALU} + t_{DMem} + t_{RWB}$

☐ At the rising edge of the following clock, the PC, the register file and the memory are updated



Pipelined DLX Datapath

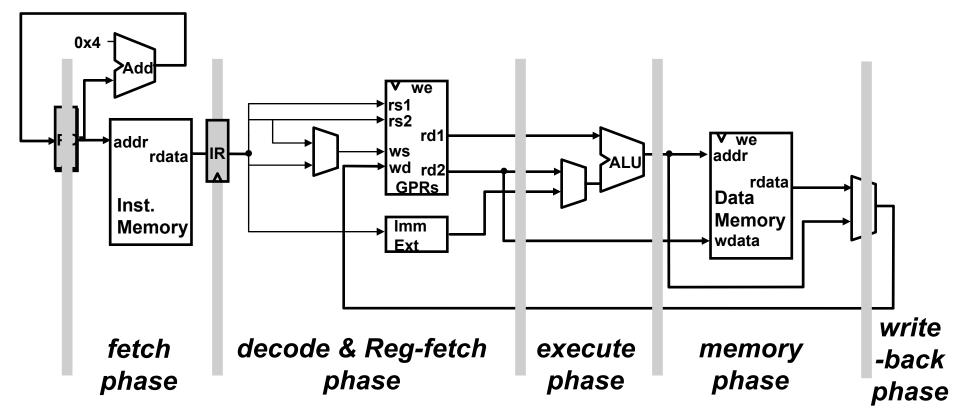


Clock period can be reduced by dividing the execution of an instruction into multiple cycles

$$t_C > max \{t_{IM}, t_{RF}, t_{ALU}, t_{DM}, t_{RW}\} = t_{DM} (probably)$$

However, CPI will increase unless instructions are pipelined



An Ideal Pipeline

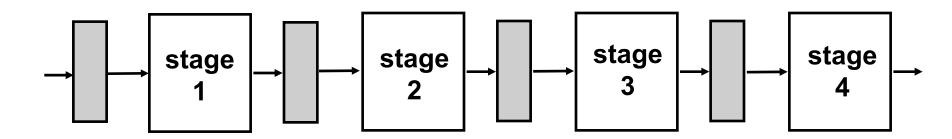

- ☐ All objects go through the same stages
- ☐ No sharing of resources between any two stages
- ☐ Propagation delay through all pipeline stages is equal
- ☐ The scheduling of an object entering the pipeline is not affected by the objects in other stages

These conditions generally hold for industrial assembly lines. An instruction pipeline, however, cannot satisfy the last condition. Why?



Pipelining History

- □ Some very early machines had limited pipelined execution (e.g., Zuse Z4, WWII)
 - Usually overlap fetch of next instruction with current execution
- □ IBM Stretch first major "supercomputer" incorporating extensive pipelining, result bypassing, and branch prediction
 - project started in 1954, delivered in 1961
 - didn't meet initial performance goal of 100x faster with 10x faster circuits
 - up to 11 macroinstructions in pipeline at same time
 - microcode engine highly pipelined also (up to 6 microinstructions in pipeline at same time)
 - Stretch was origin of 8-bit byte and lower case characters, carried on into IBM 360



How to divide the datapath into stages

Suppose memory is significantly slower than other stages. In particular, suppose


$$t_{IM} = t_{DM} = 10 \text{ units}$$

 $t_{ALU} = 5 \text{ units}$
 $t_{RF} = t_{RW} = 1 \text{ unit}$

Since the slowest stage determines the clock, it may be possible to combine some stages without any loss of performance



Minimizing Critical Path

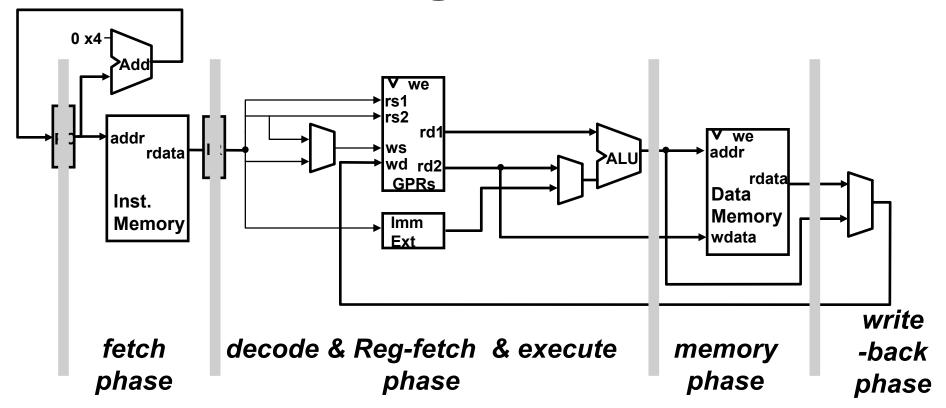

$$t_C > max \{t_{IM}, t_{RF} + t_{ALU}, t_{DM}, t_{RW}\}$$

Write-back stage takes much less time than other stages. Suppose we combined it with the memory phase

⇒ increase the critical path by 10%



Maximum Speedup by Pipelining

For the 4-stage pipeline, given

 $t_{IM} = t_{DM} = 10$ units, $t_{ALU} = 5$ units, $t_{RF} = t_{RW} = 1$ unit t_{C} could be reduced from 27 units to 10 units

 \Rightarrow speedup = 2.7

However, if $t_{IM} = t_{DM} = t_{ALU} = t_{RF} = t_{RW} = 5$ units The same 4-stage pipeline can reduce t_{C} from 25 units to 10 units

 \Rightarrow speedup = 2.5

But, since $t_{IM} = t_{DM} = t_{ALU} = t_{RF} = t_{RW}$, it is possible to achieve higher speedup with more stages in the pipeline.

A 5-stage pipeline can reduce t_c from 25 units to 5 units

 \Rightarrow speedup = 5



Technology Assumptions

We will assume

- A small amount of very fast memory (caches) backed up by a large, slower memory
- Fast ALU (at least for integers)
- Multiported Register files (slower!).


It makes the following timing assumption valid


$$t_{\text{IM}} \approx t_{\text{RF}} \approx t_{\text{ALU}} \approx t_{\text{DM}} \approx t_{\text{RW}}$$

A 5-stage pipelined Harvard-style architecture will be the focus of our detailed design



5-Stage Pipelined Execution

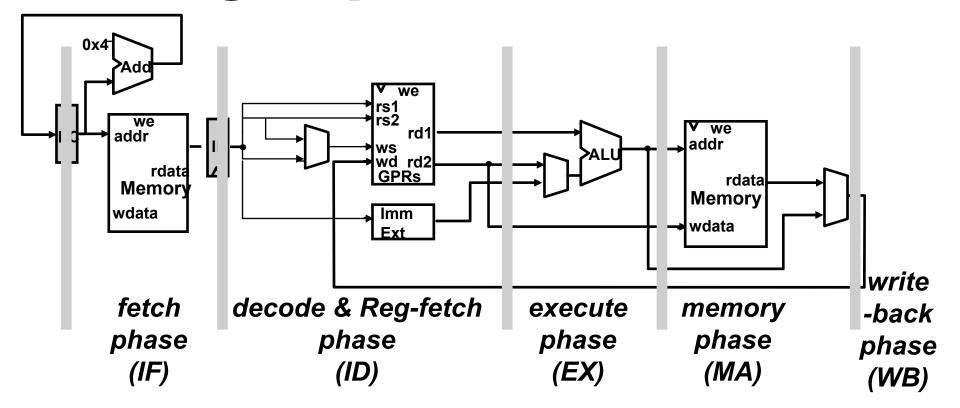


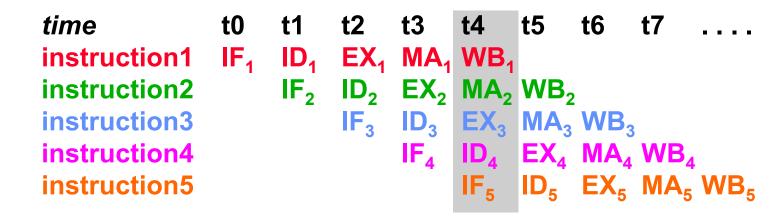


5-Stage Pipelined Execution

Asanovic/Devadas Spring 2002 6.823


Resource Usage Diagram

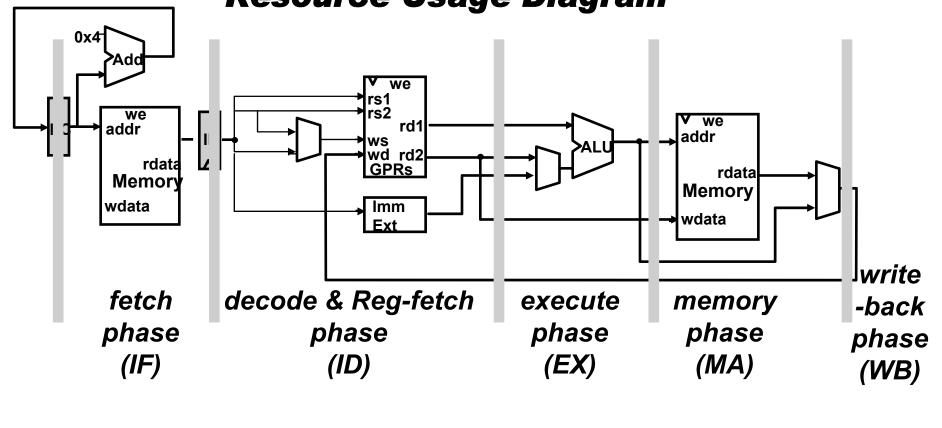

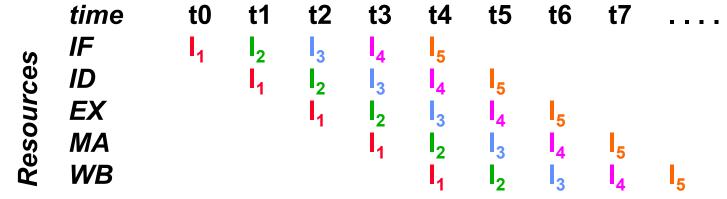




Pipelined Execution: ALU Instructions

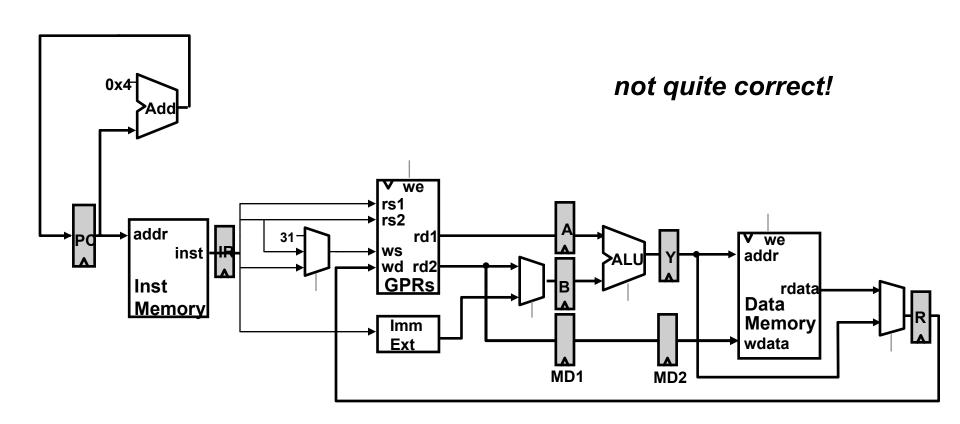




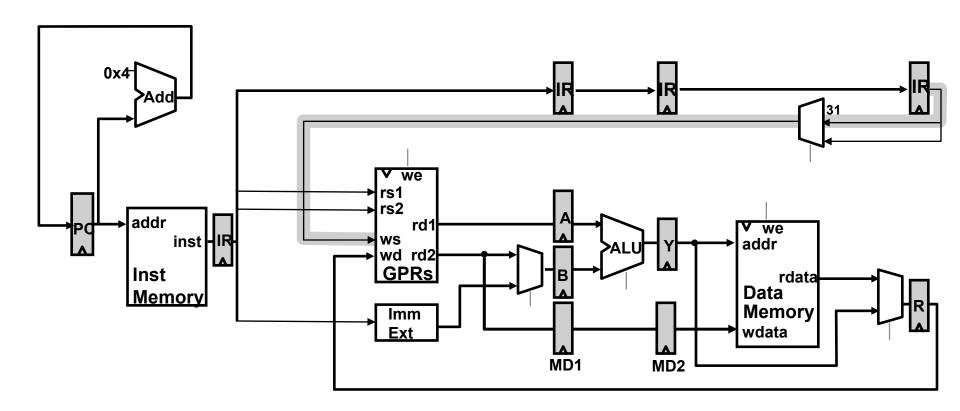Pipelined Execution: Need for Several IR's





IRs and Control points

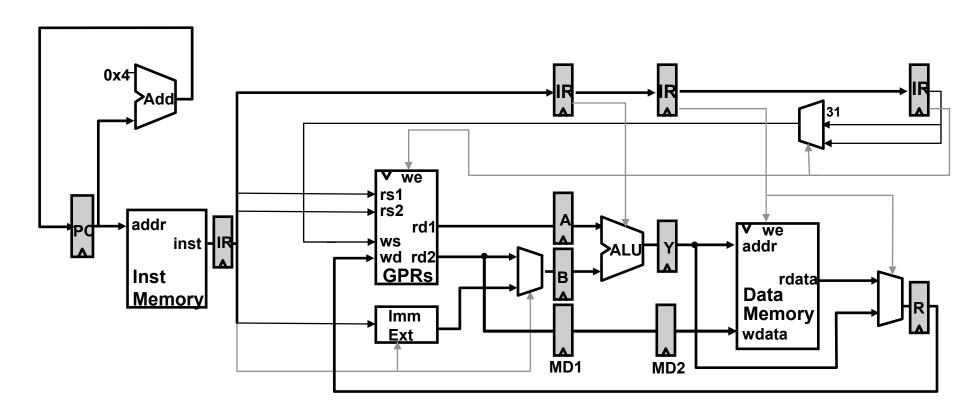


Are control points connected properly?

- Load/Store instructions
- ALU instructions



Pipelined DLX Datapath

without jumps

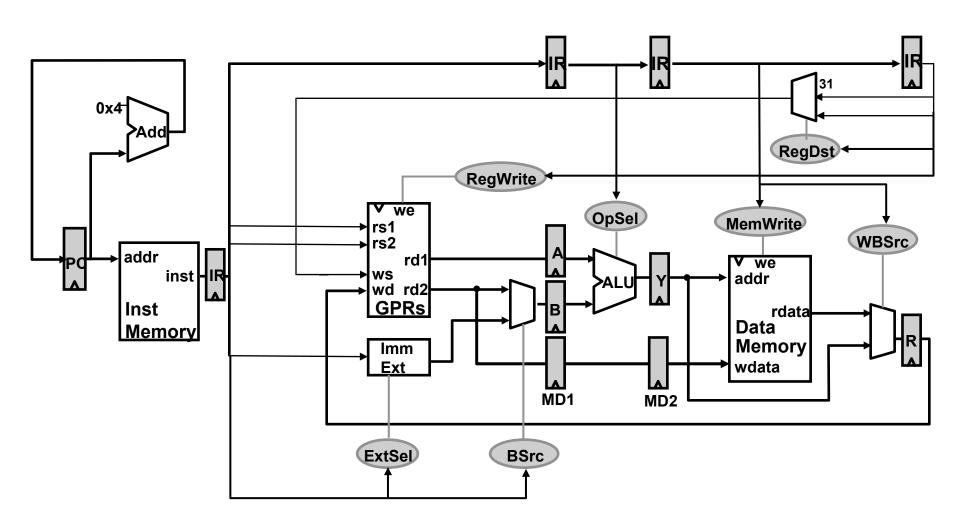




How Instructions can Interact with each other in a Pipeline

- An instruction in the pipeline may need a resource being used by another instruction in the pipeline structural hazard
- An instruction may produce data that is needed by a later instruction data hazard
- In the extreme case, an instruction may determine the next instruction to be executed control hazard (branches, interrupts,...)



Feedback to Resolve Hazards

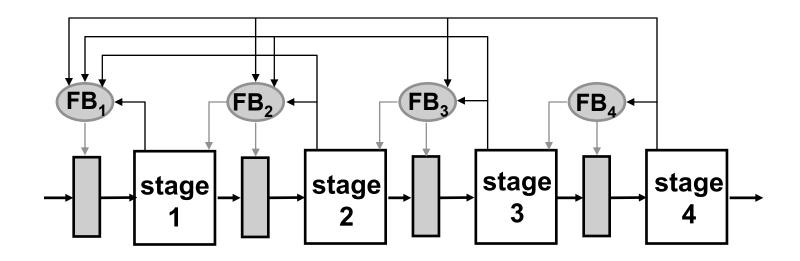

Controlling pipeline in this manner works provided the instruction at stage i+1 can complete without any interference from instructions in stages 1 to i (otherwise deadlocks may occur)

Feedback to previous stages is used to stall or kill instructions